

---

# CHAPTER 7

© 2008 Pearson Education, Inc.

---

## 7-1.

- (a)  $R1 + 2$ 's complement of  $R2 = 2^n + R1 - R2$ . If  $R1 \geq R2$ , the result is  $\geq 2^n$ . The  $2^n$  gives  $C = 1$ .  
 $R1 + 2$ 's complement of  $R2 = 2^n + R1 - R2$ , if  $R1 < R2$ , the result is  $< 2^n$  giving  $C = 0$ .
- (b) If  $C = 1$  then  $R1 \geq R2$  and there is no borrow.  
If  $C = 0$  then  $R1 < R2$  and there is a borrow. Thus, the borrow is the complement of the  $C$  status bit.

---

## 7-2. \*

1001 1001	
<u>1100 0011</u>	
1000 0001	AND
1101 1011	OR
0101 1010	XOR

---

## 7-3.

- (a) AND, 1010 1010 1010 1010      (b) OR, 0000 0000 0000 1111  
(c) XOR, 1111 1111 0000 0000

---

## 7-4. \*

sl 1001 0100                      sr 0110 0101

---

## 7-5. \*

$Q_i$  remains connected to MUX data input 0. Connect  $D_i$  to MUX data input 1 instead of Mux data input 3. Connect  $Q_{i-1}$  to MUX data input 2 instead of MUX data input 1. Finally, 0 is connected to MUX data input 3.

---

## 7-6. \*

- a) 1000, 0100, 0010, 0001, 1000. ...  
b) # States =  $n$

---

## 7-7.

- a) 000, 100, 110, 111, 011, 001, 000, ...  
b) # States =  $2n$

---

## 7-8.

- a) 8                                      b) 3


7-9.†

Examine an  $n$ -bit ripple counter and an  $n$ -bit synchronous counter. If either of these counters cycles through all of its states, there are  $2(2^n) = 2^{n+1}$  transitions for the clock, and there are  $2^{n+1} - 2$  total transitions for all flip-flop outputs. For the ripple counter, the clock transitions occur on the input of only one stage, the 0th stage. For the synchronous counter, the clock transitions occur on the inputs to all of the  $n$  stages. Combining the transition counts above, the ratio of the input + output transitions for the synchronous counter compared to the ripple counter is:


$$[n 2^{n+1} + 2^{n+1} - 2] / [2^{n+1} + 2^{n+1} - 2] \approx (n + 1) 2^{n+1} / 2 (2^{n+1}) = (n+1)/2$$

Thus, the power dissipated by the synchronous counter is at least as large as that dissipated by the ripple counter in all cases and grows more rapidly with the number of stages.


7-10.

 

7-11.

 


7-12.

 

 7-13.\*


The equations given on page 364-5 can be manipulated into SOP form as follows:  $D_1 = \bar{Q}_1$ ,  $D_2 = Q_2 \oplus Q_1\bar{Q}_8 = Q_1\bar{Q}_2\bar{Q}_8 + \bar{Q}_1Q_2 + Q_2Q_8$ ,  $D_4 = Q_4 \oplus Q_1Q_2 = Q_1Q_2\bar{Q}_4 + \bar{Q}_1Q_4 + \bar{Q}_2Q_4$ ,  $D_8 = Q_8 \oplus (Q_1Q_8 + Q_1Q_2Q_4) = \bar{Q}_8(Q_1Q_8 + Q_1Q_2Q_4) + Q_8(\bar{Q}_1 + \bar{Q}_8)(\bar{Q}_1 + \bar{Q}_2 + \bar{Q}_4) = Q_1Q_2Q_4\bar{Q}_8 + \bar{Q}_1Q_8$ . These equations are mapped onto the K-maps for Table 7-9 below and meet the specifications given by the maps and the table.



To add the enable, change D1 to:

$$D_1 = Q_1 \oplus EN.$$

 For the other three functions, AND EN with the expression XORed with the state variable. The circuit below results.



7-14.\*

Present state			Next state		
A	B	C	A	B	C
	0	0		0	1
	0	1		1	0
	1	0		0	0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0

a)  $D_B = C$       b)  $D_A = BC + A\bar{C}$   
 $D_C = \bar{B}\bar{C}$        $D_B = \bar{A}\bar{B}C + B\bar{C}$   
 $D_C = \bar{C}$

7-15.

Present state			Next state		
A	B	C	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	0	0	0


$$D_A = A\bar{B} + A\bar{C} + \bar{A}BC$$

$$D_B = \bar{B}$$


$$D_C = \bar{B}C + B\bar{C}$$

 7-16.


The basic cell of the register is as follows:




7-17.\*

 


7-18.

 


7-19.\*

 

 
**7-20.** (Errata: Change “register A” to “register B”)




**7-21.**

 


**7-22.**

 

7-23.

 


7-24.\*

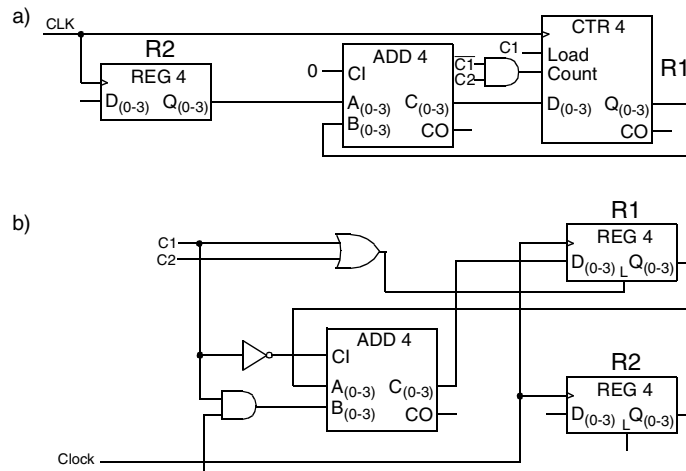


7-25.

The register transfer logic is as follows:

Operation	Select		Load		
	S1	S0	L0	L1	L2
CA: R1 ← R0	0	0	0	1	0
CB: R0 ← R1, R2 ← R0	0	1	1	0	1
CC: R1 ← R2, R0 ← R2	1	0	1	1	0

 


## Problem Solutions – Chapter 7

 

**7-26.**


Replace multiplexer with:

 

**7-27.\***


- |   |   |
|---|---|
| <p>a) Destination <math>\leftarrow</math> Source Registers</p> <p>R0 <math>\leftarrow</math> R1, R2<br/> R1 <math>\leftarrow</math> R4<br/> R2 <math>\leftarrow</math> R3, R4<br/> R3 <math>\leftarrow</math> R1<br/> R4 <math>\leftarrow</math> R0, R2</p> | <p>b) Source Registers <math>\rightarrow</math> Destination</p> <p>R0 <math>\rightarrow</math> R4<br/> R1 <math>\rightarrow</math> R0, R3<br/> R2 <math>\rightarrow</math> R0, R4<br/> R3 <math>\rightarrow</math> R2<br/> R4 <math>\rightarrow</math> R1, R2</p> |
|---|---|

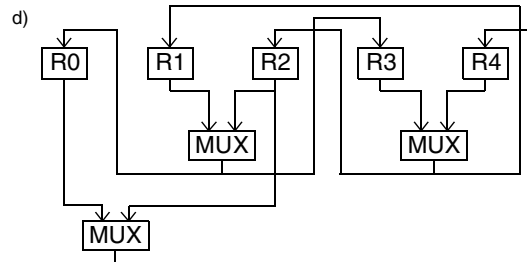c) The minimum number of buses needed for operation of the transfers is three since transfer Cb requires three different sources.




**7-28.**

 a) Using two clock cycles, the minimum # of buses is 2 .



7-29.

Two clock cycles minimum

 

7-30.\*


0101, 1010, 0101, 1010, 1101, 0110, 0011, 0001, 1000

7-31.\*

Shifts:	0	1	2	3	4
A	0111	0011	0001	1000	1100
B	0101	0010	0001	0000	0000
C	0	1	1	1	0

7-32.\*

Default: Z1 = 0, Z2 = 0

 

7-33.\*

State: STA, STA, STB, STC, STA, STB, STC, STA, STB

Z: 0, 0, 1, 1, 0, 0, 1, 0, -

7-34.


State	Input	Next State	Output
STA	$\overline{W}$	STA	*
STA	W	STB	*
STB	$\overline{X} Y$	STA	*
STB	X	STC	*
STB	$\overline{X} \overline{Y}$	STC	Z
STC		STA	Z

\*Default: Z = 0




7-35.

Default:  $Z = 0$

 


7-36.\*

Default:  $Z = 0$

 

7-37.†

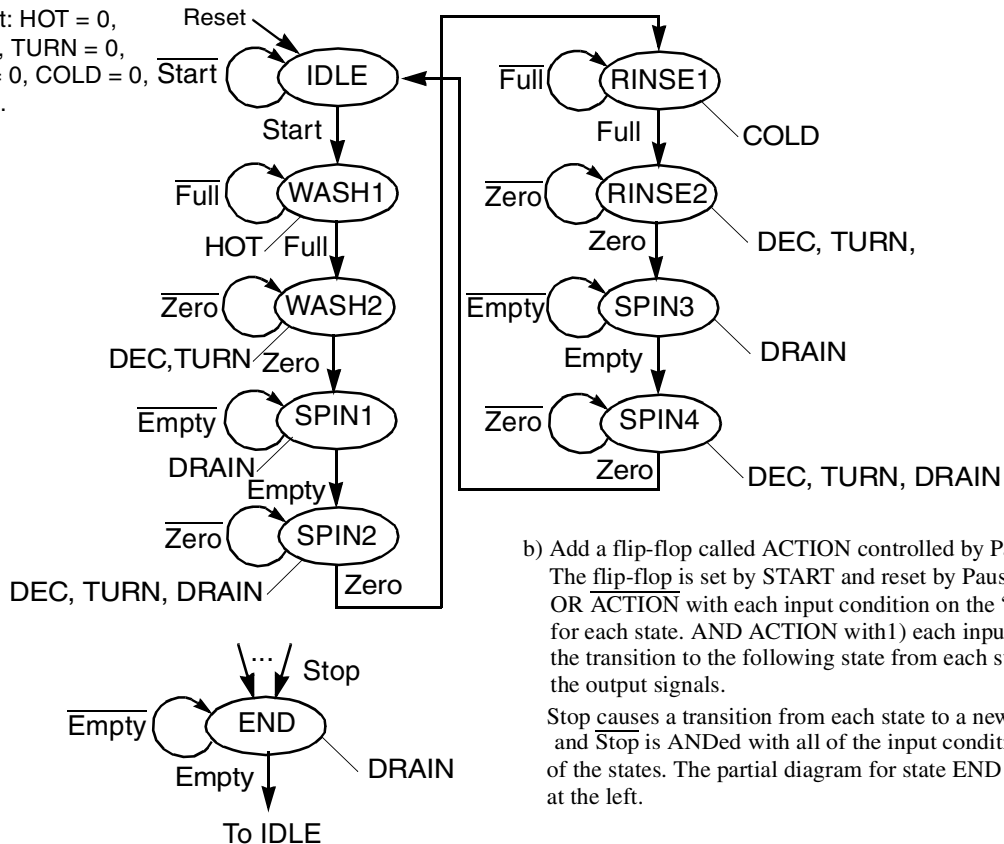a) Default: HOT = 0,  
DEC = 0, TURN = 0,  
DRAIN = 0, COLD = 0,  
Load = 0.




b) Add a flip-flop called ACTION controlled by Pause and Start. The flip-flop is set by START and reset by Pause. OR ACTION with each input condition on the “loop” for each state. AND ACTION with 1) each input condition on the transition to the following state from each state and 2) all the output signals.

Stop causes a transition from each state to a new state END and Stop is ANDed with all of the input conditions on each of the states. The partial diagram for state END appears at the left.

 7-38.

Default: GN = 0, RE = 0,  
YN = 0, RN = 0, GE = 0,  
YE = 0



7-39.\*

	Present state			Input	Next state			Output
	A	B	C		A	B	C	
STA	1	0	0	$\bar{W}$	1	0	0	
	1	0	0	W	0	1	0	
STB	0	1	0	$\bar{X}Y$	1	0	0	
	0	1	0	X	0	0	1	
	0	1	0	$\bar{X}\bar{Y}$	0	0	1	Z
STC	0	0	1		1	0	0	Z

$$D_A = A\bar{W} + B\bar{X}Y + C$$

$$D_B = AW$$

$$D_C = B(X + \bar{Y})$$


$$Z = B\bar{X}\bar{Y} + C$$

The implementation consists of the logic represented by the above equations and three D flip-flops with Reset connected to S on the first flip-flop and to R on the other two flip-flops.

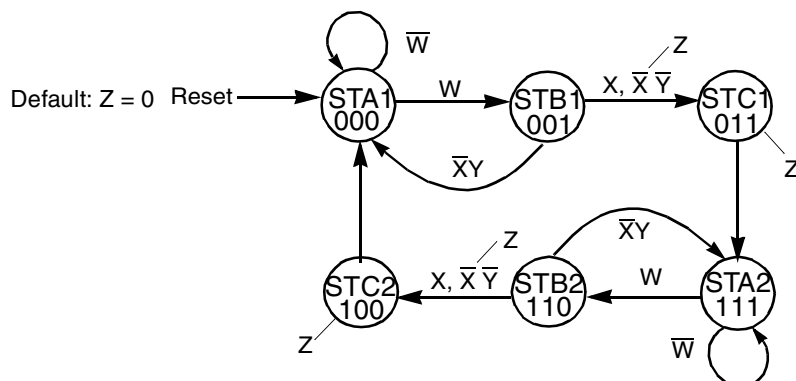7-40.


This state diagram has a closed loop of three transitions (STA to STB to STC to STA). In a Gray code, only one bit may change in going from one state to another. Any state machine diagram with a loop of an odd number of transitions is impossible to encode with a Gray code. For example, to go from STA to STB suppose bit B1 of the code changes. Then to go from STB to STC, some other bit, say B2 must change. Since two bits have changed, it is impossible to return to state STA. Thus, the answer to this problem is that this state diagram cannot be implemented with a Gray code.

But suppose that we use two equivalent states to represent each of the original states, STA1, STB1, STC1, STA2, STB2, and STC2. Is it possible to implement the new diagram generated such that it has exactly the same properties as the old diagram. Suppose that the codes are 000, 001, 011, 111, 110, 100, respectively, for the six states. The coded diagram is:



The behavior of this diagram is the same as that of the original and it has been successfully Gray coded by assigning two codes to each state. The implementation is a straightforward design problem with two unused states.

7-41.

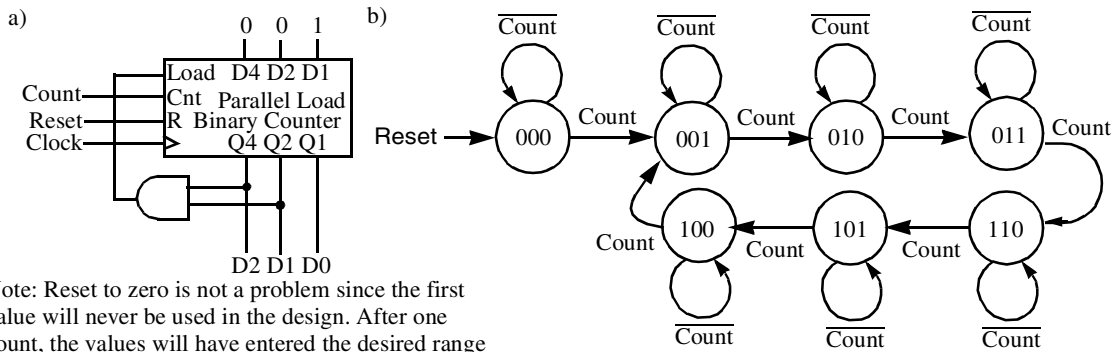

Note: Reset to zero is not a problem since the first value will never be used in the design. After one count, the values will have entered the desired range of 1 through 6.

Applying K-maps to the table entries:

State	Cnt = 0	Cnt = 1
000	000	001
001	001	010
010	010	011
011	011	100
100	100	101
101	101	110
110	110	111
111	ddd	ddd

$$D_{Q4} = Q4 \overline{C} + Q4 \overline{Q2} + Q1 Q2 C$$

$$D_{Q2} = Q2 \overline{C} + Q1 Q2 C + \overline{Q4} Q2 \overline{Q1}$$

$$D_{Q1} = Q1 \overline{C} + \overline{Q1} C$$

Cost comparison:



$$a) 3(14 + 2 + 8 + 6) + 1 + 2 = 93$$

$$b) 3(14) + 4 + 6 + 11 + 10 = 73$$

The gate input cost of b) is 78.5 % that of a).

7-42.

  a)  $DE1 = \overline{D4} \overline{D2} D1$



This circuit can be easily derived by describing the range of values greater than or equal to 100 in terms of powers of 2. The smallest value is  $2^6 + 2^5 + 2^2$  and the largest value is  $2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1$ . This range of D can be described by saying that  $2^6$  and  $2^5$  must be present and any of  $2^2$ ,  $2^3$ , or  $2^4$  must be present in D. The resulting equation is  $D6 D5 (D4 + D3 + D2)$ . An alternative way of finding this is to contract the carry circuit for  $D + 2$ 's comp of 1100100.

7-43.

Binary	BCD ( $C_0 = 0$ )	BCD ( $C_0 = 1$ )	
$B_3B_2B_1B_0$	$C_4D_3D_2D_1D_0$	$C_4D_3D_2D_1D_0$	
0000	00000	00001	For $C_0 = 0$ ,
0001	00001	00010	$C4 = B3 \overline{B2} + B3 B1$
0010	00010	00011	$D3 = B3 \overline{B2} \overline{B1}$
0011	00011	00100	$D2 = \overline{B3} B2 + B2 B1$
0100	00100	00101	$D1 = \overline{B3} B1 + B3 B2 \overline{B1}$
0101	00101	00110	$D0 = B0$
0110	00110	00111	For $C_0 = 1$ ,
0111	00111	01000	$C4 = B3 \overline{B2} + B3 B1 + B3 B0$
1000	01000	01001	$D3 = B3 \overline{B2} \overline{B1} \overline{B0} + \overline{B3} B2 B1 B0$
1001	01001	10000	$D2 = \overline{B3} B2 \overline{B1} + B3 B2 B0 + B2 B1 \overline{B0} + \overline{B3} \overline{B2} B1 B0$
1010	10000	10001	$D1 = \overline{B3} \overline{B1} B0 + \overline{B3} B1 \overline{B0} + B3 B1 B0 + B3 B2 \overline{B1} \overline{B0}$
1011	10001	10010	$D0 = \overline{B0}$
1100	10010	10011	Combining,
1101	10011	10100	$C4 = \overline{C0} (B3 \overline{B2} + B3 B1) + C0 (B3 \overline{B2} + B3 B1 + B3 B0)$
1110	10100	10101	$D3 = \overline{C0} (B3 \overline{B2} \overline{B1}) + C0 (B3 \overline{B2} \overline{B1} \overline{B0} + \overline{B3} B2 B1 B0)$
1111	10101	10110	$D2 = \overline{C0} (\overline{B3} B2 + B2 B1) + C0 (\overline{B3} B2 \overline{B1} + B3 B2 B0 + B2 B1 \overline{B0} + \overline{B3} \overline{B2} B1 B0)$
			$D1 = \overline{C0} (\overline{B3} B1 + B3 B2 \overline{B1}) + C0 (\overline{B3} \overline{B1} B0 + \overline{B3} B1 \overline{B0} + B3 B1 B0 + B3 B2 \overline{B1} \overline{B0})$
			$D0 = \overline{C0} B0 + C0 \overline{B0}$
			Optimizing,
			$C4 = B3 (B2 + B1 + C0 B0)$
			$D3 = (\overline{C0} + \overline{B0}) B3 \overline{B2} \overline{B1} + C0 \overline{B3} B2 B1 B0$
			$D2 = B2 (\overline{C0} B1 + \overline{B3} \overline{B1} + B1 \overline{B0} + C0 B3 B0) + C0 \overline{B3} \overline{B2} B1 B0$
			$D1 = (\overline{C0} + \overline{B0}) B3 B2 \overline{B1} + \overline{C0} \overline{B3} B1 + C0 B0 (B3 B1 + \overline{B3} \overline{B1}) + \overline{B3} B1 \overline{B0}$
			$D0 = \overline{C0} B0 + C0 \overline{B0}$

7-44.

a) Transition constraint checking for Figure 7-28.

Constraint 1:		Constraint 2:	
INIT: No possible conflicts since a single transition.		Condition implicitly = 1	OK
BEGIN: $\overline{ROLL} \cdot ROLL = 0$	OK	BEGIN: $\overline{ROLL} + ROLL = 1$	OK
ROL: $ROLL \cdot \overline{ROLL} = 0$	OK	ROL: $ROLL + \overline{ROLL} = 1$	OK
ONE: $DIE1 \cdot \overline{DIE1} = 0$	OK	DIE1 + $\overline{DIE1} = 1$	OK
ROH: $ROLL \cdot \overline{ROLL} \cdot HOLD = 0$	OK	ROH: $ROLL + \overline{ROLL} \cdot HOLD + \overline{ROLL} \cdot \overline{HOLD} = 1$	OK
$ROLL \cdot \overline{ROLL} \cdot \overline{HOLD} = 0$	OK		
$\overline{ROLL} \cdot HOLD \cdot \overline{ROLL} \cdot \overline{HOLD} = 0$	OK		
TEST: $WN \cdot \overline{WN} = 0$	OK	TEST: $WN + \overline{WN} = 1$	OK
WIN: $NEW\_GAME \cdot \overline{NEW\_GAME} = 0$	OK	WIN: $NEW\_GAME + \overline{NEW\_GAME} = 1$	OK

b) Implementation of state machine diagram Figure 7-28 using 1-hot code.

The order from LSB to MSB for the state variables is the same as the order of the states in the diagram from top to bottom. The state variables have the same respective names as the states, e.g., INIT, BEGIN, ...

The flip-flop input equations:

$$\begin{aligned}
 D_{INIT} &= INIT(t+1) = WIN \cdot NEW\_GAME \\
 D_{BEGIN} &= BEGIN(t+1) = INIT + ONE \cdot DIE1 + TEST \cdot \overline{WN} + BEGIN \cdot \overline{ROLL} \\
 D_{ROL} &= BEGIN \cdot ROLL + ROH \cdot ROLL + ROL \cdot ROLL \\
 D_{ONE} &= ROL \cdot \overline{ROLL} \\
 D_{ROH} &= ONE \cdot \overline{DIE1} + ROH \cdot \overline{ROLL} \cdot \overline{HOLD} \\
 D_{TEST} &= ROH \cdot \overline{ROLL} \cdot HOLD \\
 D_{WIN} &= TEST \cdot WN + WIN \cdot \overline{NEW\_GAME}
 \end{aligned}$$


The output equations:

$$\begin{aligned}
 RST1 &= INIT, RST2 = INIT, CPFI = INIT, LDCP = INIT + TEST \cdot \overline{WN} + ONE \cdot DIE1, RSSU = BEGIN, ENDI = ROL, LDSU \\
 &= ONE, LDT1 = ROH \cdot \overline{CP} \cdot \overline{ROLL} \cdot HOLD, LDT2 = ROH \cdot CP \cdot \overline{ROLL} \cdot HOLD, BP1 = WIN \cdot \overline{CP}, BP2 = WIN \cdot CP
 \end{aligned}$$



The circuit consists of gates implementing the above equations with logic shared where possible, and seven D flip-flops. The flip-flop for INIT has Reset attached to S and the remaining flip-flops have Reset attached to R.

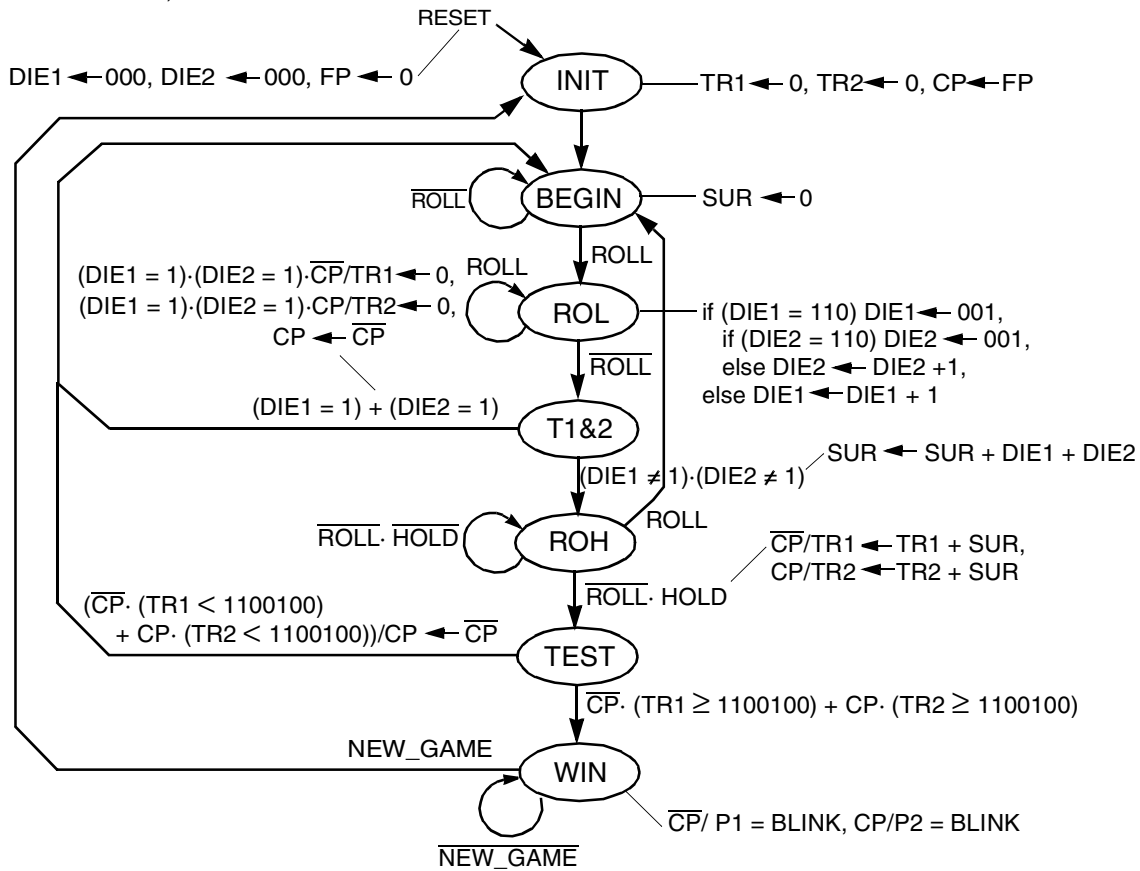
7-45.†

Default:  $P1 = \overline{CP}$ ,  $P2 = CP$



7-46.\*

  

 

```


    C[0] = EN,
    C[1] = C[0] & Q[0],
    C[2] = C[1] & Q[1],
    C[3] = C[2] & Q[2],
    CO = C[3] & Q[3];

assign
    D_in[0] = C[0] ^ Q[0],
    D_in[1] = C[1] ^ Q[1],
    D_in[2] = C[2] ^ Q[2],
    D_in[3] = C[3] ^ Q[3];

dff_v
    g1(Clock, Reset, D_in[0], Q[0]),
    g2(Clock, Reset, D_in[1], Q[1]),
    g3(Clock, Reset, D_in[2], Q[2]),
    g4(Clock, Reset, D_in[3], Q[3]);

endmodule

```

 

7-48.\*

```

library IEEE;
use IEEE.std_logic_1164.all;


entity reg_4_bit is
  port (
    CLEAR, CLK: in STD_LOGIC;
    D: in STD_LOGIC_VECTOR (3 downto 0);
    Q: out STD_LOGIC_VECTOR (3 downto 0)
  );
end reg_4_bit;

architecture reg_4_bit_arch of reg_4_bit is
begin

  process (CLK, CLEAR)
  begin
    if CLEAR = '0' then                --asynchronous RESET active Low
      Q <= "0000";
    elsif (CLK'event and CLK='1') then  --CLK rising edge
      Q <= D;
    end if;
  end process;

end reg_4_bit_arch;

```

 

7-49.

```

library IEEE;
use IEEE.std_logic_1164.all;

entity reg_4_bit is
  port (
    LOAD, CLK: in STD_LOGIC;
    D: in STD_LOGIC_VECTOR (3 downto 0);
    Q: out STD_LOGIC_VECTOR (3 downto 0)
  );
end reg_4_bit;


-- (continued in next column)

architecture reg_4_bit_load_arch of reg_4_bit is
begin

  process (CLK)
  begin
    if (CLK'event and CLK='1') then --CLK rising edge
      if LOAD = '1' then
        Q <= D;
      end if;
    end if;
  end process;

endreg_4_bit_load_arch;

```

 

7-50.

```

library ieee;
use ieee.std_logic_1164.all;
entity dff is
    port(CLK, RESET, D: in std_logic;
          Q: out std_logic);
end dff;

architecture pet_pr of dff is
    -- Implements positive edge-triggered bit state storage
    -- with asynchronous reset.
    signal state: std_logic;
begin
    Q <= state;
    process (CLK, RESET)
    begin
        if (RESET = '1') then
            state <= '0';
        else
            if (CLK'event and CLK = '1') then
                state <= D;
            end if;
        end if;
    end process;
end;

library IEEE;
use IEEE.std_logic_1164.all;
entity counter_4_bit is
    port (
        Clock, Reset, EN: in STD_LOGIC;
        Q: out STD_LOGIC_VECTOR (3 downto 0);
        CO: out STD_LOGIC
    );
end counter_4_bit;

```

```


architecture counter_4_bit_arch of counter_4_bit is
    component dff
        port(CLK, RESET, D: in std_logic;
              Q: out std_logic
            );
    end component ;
    signal D_in, C, Q_out: std_logic_vector(3 downto 0);
begin
    C(0) <= EN;
    C(1) <= C(0) and Q_out(0);
    C(2) <= C(1) and Q_out(1);
    C(3) <= C(2) and Q_out(2);
    CO <= C(3) and Q_out(3);

    D_in(0) <= C(0) xor Q_out(0);
    D_in(1) <= C(1) xor Q_out(1);
    D_in(2) <= C(2) xor Q_out(2);
    D_in(3) <= C(3) xor Q_out(3);

    bit0: dff
        port map (Clock, Reset, D_in(0), Q_out(0));
    bit1: dff
        port map (Clock, Reset, D_in(1), Q_out(1));
    bit2: dff
        port map (Clock, Reset, D_in(2), Q_out(2));
    bit3: dff
        port map (Clock, Reset, D_in(3), Q_out(3));

    Q <= Q_out;
end counter_4_bit_arch;

```

 


7-51.\*

```

module register_4_bit (D, CLK, CLR, Q) ;
    input [3:0] D ;
    input CLK, CLR ;
    output [3:0] Q ;
    reg [3:0] Q ;

    always @(posedge CLK or negedge CLR)
    begin
        if (~CLR)
            Q = 4'b0000;      //asynchronous RESET active low
        else
            Q = D;             //use CLK rising edge
        end if;
    end
endmodule

```

 



**7-52.**


```

module register_4_bit_load (D, CLK, LOAD, Q) ;

input [3:0] D ;
input CLK, LOAD ;
output [3:0] Q ;
reg [3:0] Q ;

always @(posedge CLK)
begin
    if (LOAD)
        Q = D;
end
endmodule

```

 

**7-53.\***

```

library IEEE;
use IEEE.std_logic_1164.all;
entity prob_7_53 is
    port (clk, RESET, W, X, Y : in STD_LOGIC;
          Z : out STD_LOGIC);
end prob_7_53;

architecture process_3 of prob_7_53 is
    type state_type is (STA, STB, STC);
    signal state, next_state: state_type;
begin
    -- Process 1 - state register
    state_register: process (clk, RESET)
    begin
        if (RESET = '1') then
            state <= STA;
        else if (CLK'event and CLK='1') then
            state <= next_state;
        end if;
    end process;

    -- Process 2 - next state function
    next_state_func: process (W, X, Y, state)
    begin
        case state is
            when STA =>
                -- Continued in next column
                if W = '1' then
                    next_state <= STB;
                else
                    next_state <= STA;
                end if;
            when STB =>
                if X = '0' and Y = '1' then
                    next_state <= STA;
                else
                    next_state <= STC;
                end if;
            when STC =>
                next_state <= STA;
        end case;
    end process;

    -- Process 3 - output function
    output_func: process (X, Y, state)
    begin
        case state is
            when STA =>
                Z <= '0';
            when STB =>
                if X = '0' and Y = '0' then
                    Z <= '1';
                else
                    Z <= '0';
                end if;
            when STC =>
                Z <= '1';
        end case;
    end process;
end process_3;

```

### 7-54.\*

```
// State Diagram in Figure 5-40 using Verilog
module prob_7_54 (clk, RESET, W, X, Y, Z);
input clk, RESET, W, X, Y;
output Z;

reg[1:0] state, next_state;
parameter STA = 2'b00, STB = 2'b01, STC = 2'b10;
reg Z;

// State Register
always@(posedge clk or posedge RESET)
begin
if (RESET == 1)
state <= STA;
else
state <= next_state;
end

// Next StateFunction
always@(W or X or Y or state)
begin
case (state)
STA: if (W == 1)
next_state <= STB;
else
// (continued in the next column)
next_state <= STA;
STB: if (X == 0 & Y == 1)
next_state <= STA;
else
next_state <= STC;
STC:
next_state <= STA;
endcase
end

// Output Function
always@(X or Y or state)
begin
Z <= 0;
case (state)
STB: if (X == 0 & Y == 0)
Z <= 1;
else
Z <= 0;
STC:
Z <= 1;
endcase
end
endmodule
```